

Name of the Student: _____


Max. Marks : 24 Marks

Time : 24 Minutes

Q1.

Figure 1 shows an oscilloscope connected across resistor R which is in series with an ac supply. The supply provides a sinusoidal output of peak voltage 15 V.

Figure 1

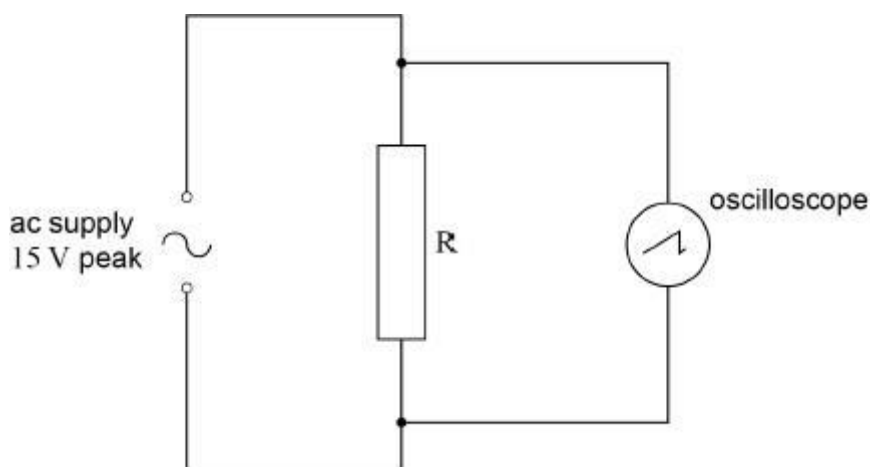


- (a) Calculate the rms voltage of the supply.

rms voltage = _____ V
(1)

Figure 2 shows the trace of the waveform displayed on the oscilloscope.

Figure 2

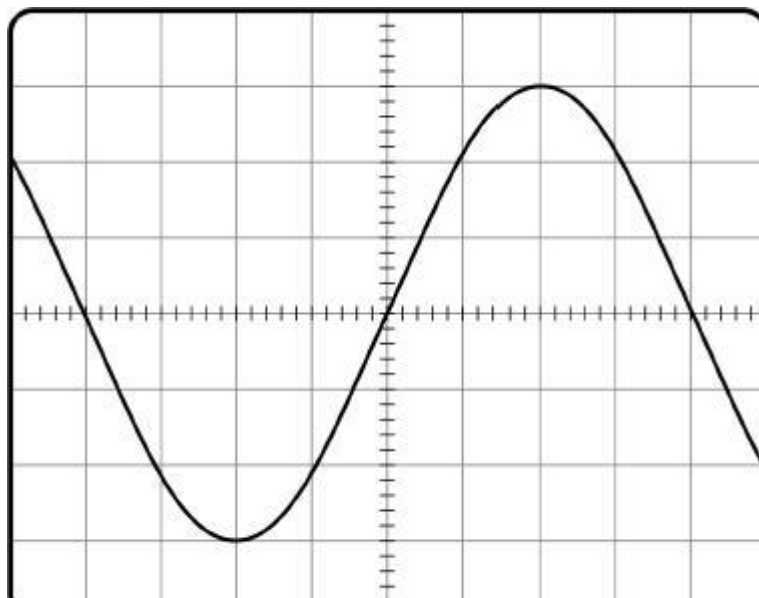

- (b) Determine the y-voltage gain of the oscilloscope used for **Figure 2**.

y-voltage gain = _____ V div⁻¹ (1)

- (c) A dc supply gives the same rate of energy dissipation in R as the ac supply in **Figure 1**.


Draw the trace of the output of the dc supply on **Figure 2**.
The oscilloscope settings remain the same.

(1)

- (d) The ac supply shown in **Figure 1** is replaced with a square-wave generator operating between 0 and +15 V.

Figure 3 shows the trace of the new waveform displayed on the oscilloscope. The time-base is set to $5.0 \times 10^{-4} \text{ s div}^{-1}$.

Figure 3

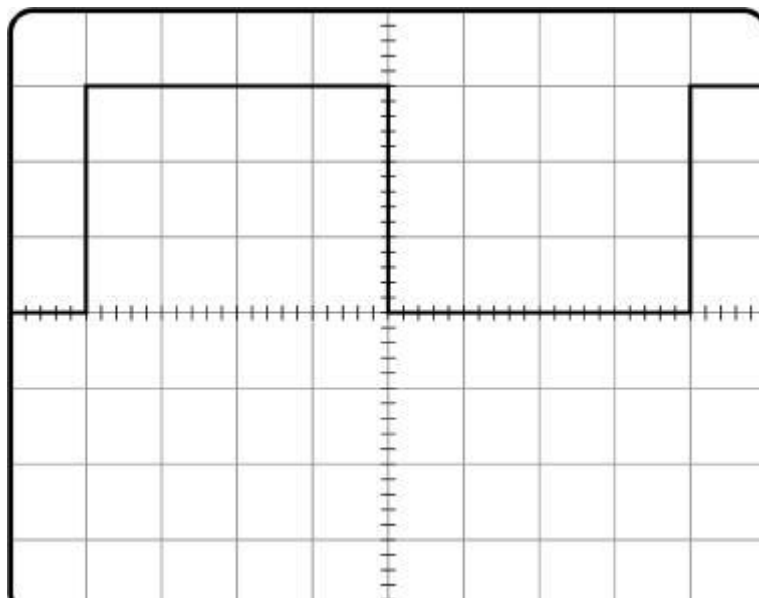


Calculate the frequency of the square waves.

frequency = _____ Hz

(1)

- (e) **Figure 4** shows the arrangement with the square-wave generator connected to an RC circuit. A capacitor C is placed in series with the resistor R . The oscilloscope is connected across the capacitor C .


Figure 4

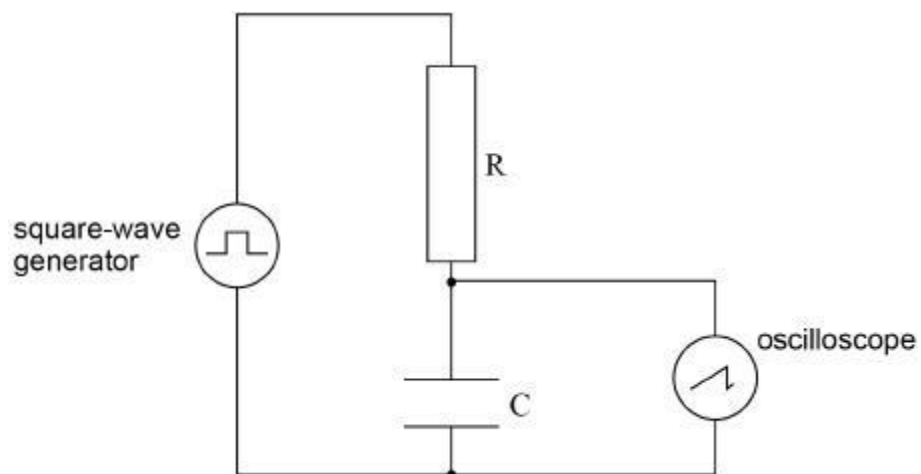

The capacitor charges and discharges.

Figure 5 shows the trace of the waveform displayed on the oscilloscope. The settings of the oscilloscope remain the same as in part (d).

Figure 5

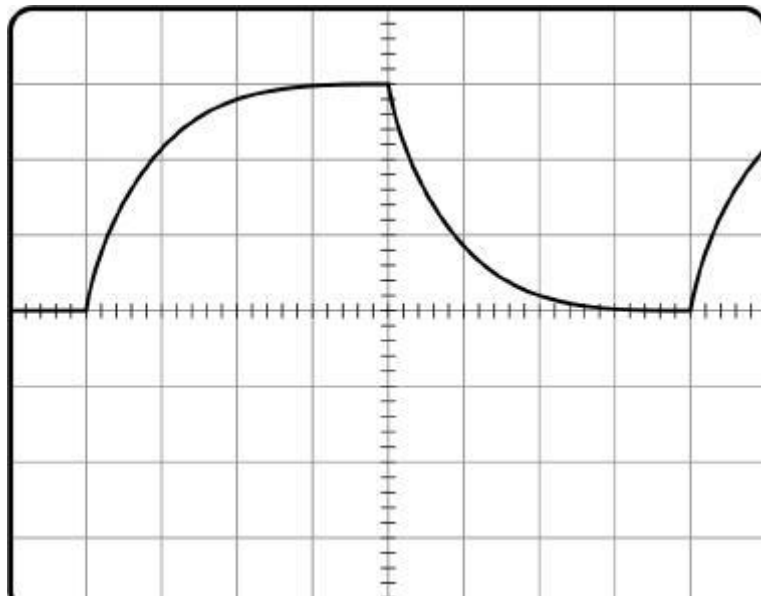

Deduce the time constant for the RC circuit, explaining each step of your method.

time constant = _____ s

(3)


- (f) State and explain a change to **one** control setting on the oscilloscope that would reduce the uncertainty in the value of the time constant.

Q2.

A simple pendulum performs oscillations of period T in a vertical plane.

Figure 1 shows views of the pendulum at the equilibrium position and at the instant of release.

Figure 1 also shows a rectangular card marked with a vertical line.

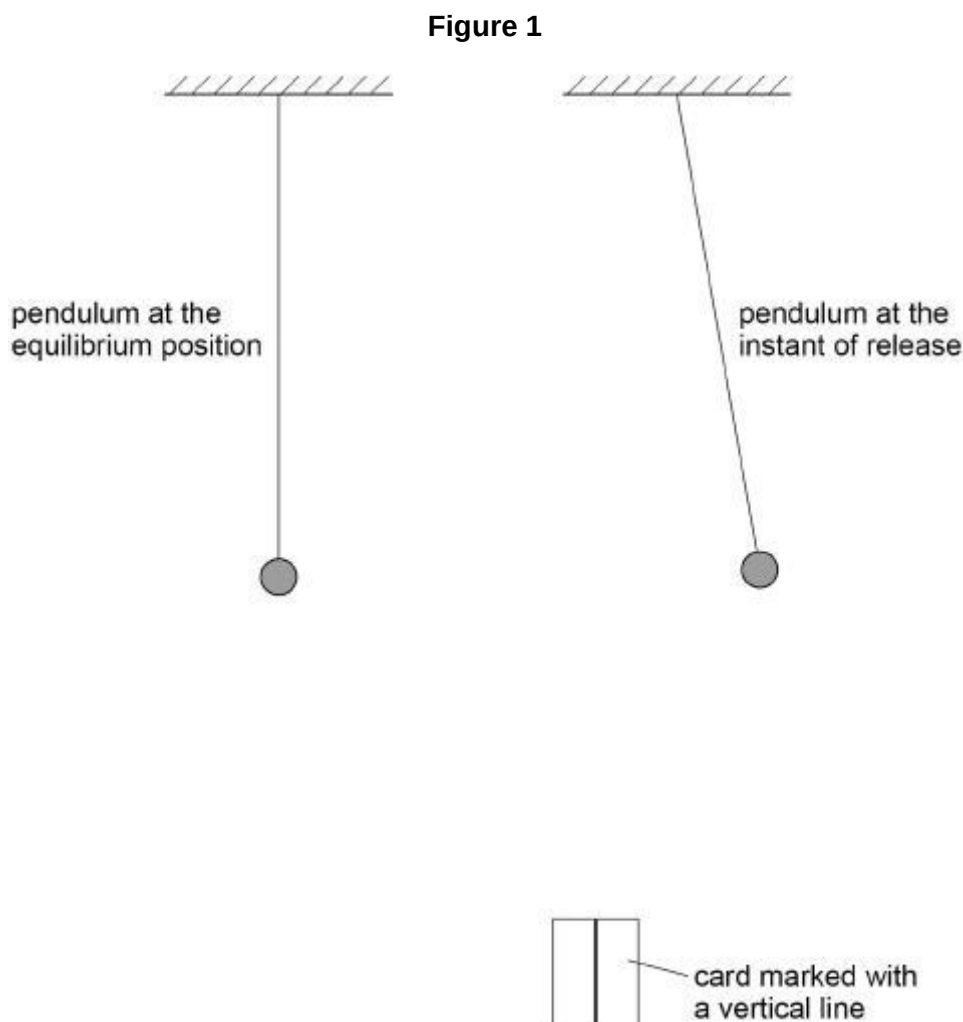


- (a) The card can be used as a fiducial mark to reduce uncertainty in the measurement of T .

Annotate **Figure 1** to show a suitable position for the fiducial mark. Explain why you chose this position.

(2)

- (b) The period of the pendulum is constant for small-amplitude oscillations.
Figure 2 shows an arrangement used to determine the maximum amplitude that can be considered to be small, by investigating how T varies with amplitude.

Figure 2

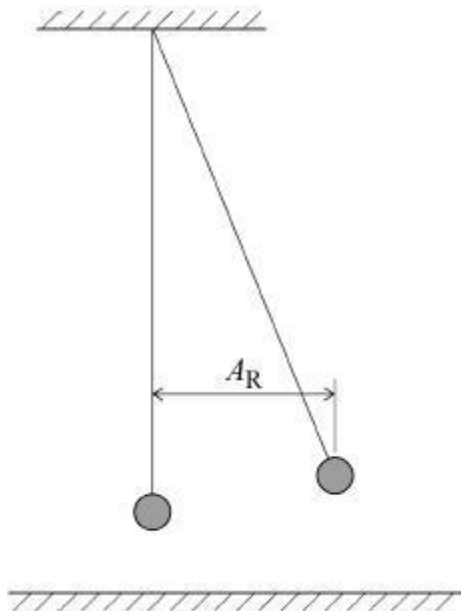


Describe a suitable procedure to determine A_R , the amplitude of the pendulum as it is released. You may add detail to **Figure 2** to illustrate your answer.

(2)

(c) **Figure 3** shows some of the results of the experiment.

Figure 3

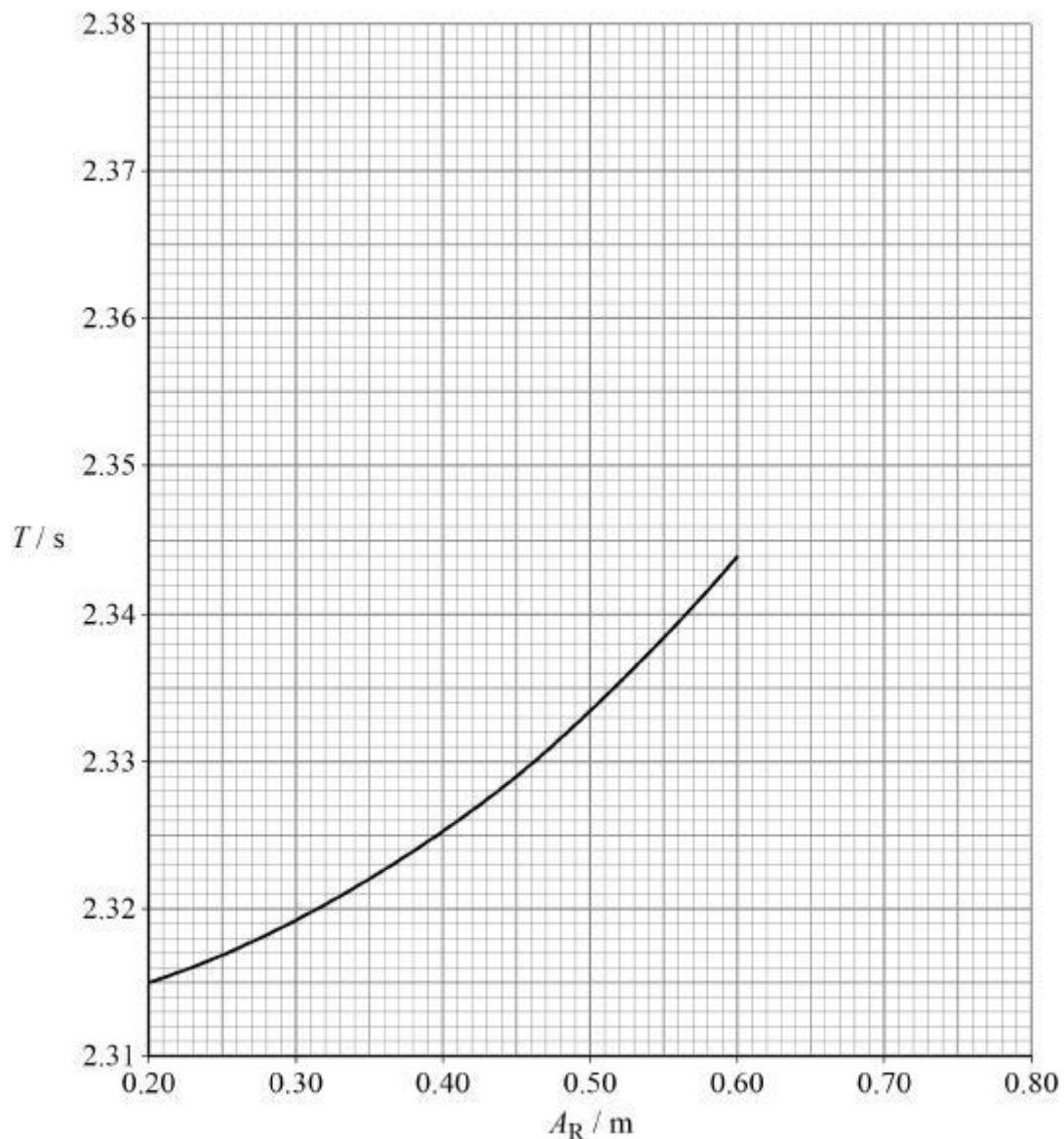

Estimate, using **Figure 3**, the expected percentage increase in T when A_R increases from 0.35 m to 0.70 m.
Show your working.

percentage increase = _____ %

(3)

In another experiment the pendulum is released from a fixed amplitude.
The amplitudes A_n of successive oscillations are recorded, where $n = 1, 2, 3, 4, 5 \dots$.

Table 1 shows six sets of readings for the amplitude A_5 .

Table 1

A_5 / m	0.217	0.247	0.225	0.223	0.218	0.224
------------------	-------	-------	-------	-------	-------	-------

(d) Determine the result that should be recorded for A_5 .

Go on to calculate the percentage uncertainty in this result.

$$A_5 = \text{_____ m}$$

$$\text{percentage uncertainty} = \text{_____ \%}$$

(3)

- (e) **Table 2** shows results for A_n and the corresponding value of $\ln(A_n / m)$ for certain values of n .

Table 2

n	A_n / m	$\ln(A_n / m)$
2	0.238	-1.435
4	0.225	
7	0.212	-1.551
10	0.194	-1.640
13	0.183	-1.698


Complete **Table 2**.

(1)

- (f) Plot on **Figure 4** a graph of $\ln(A_n / m)$ against n .

Figure 4

$\ln(A_n / \text{m})$

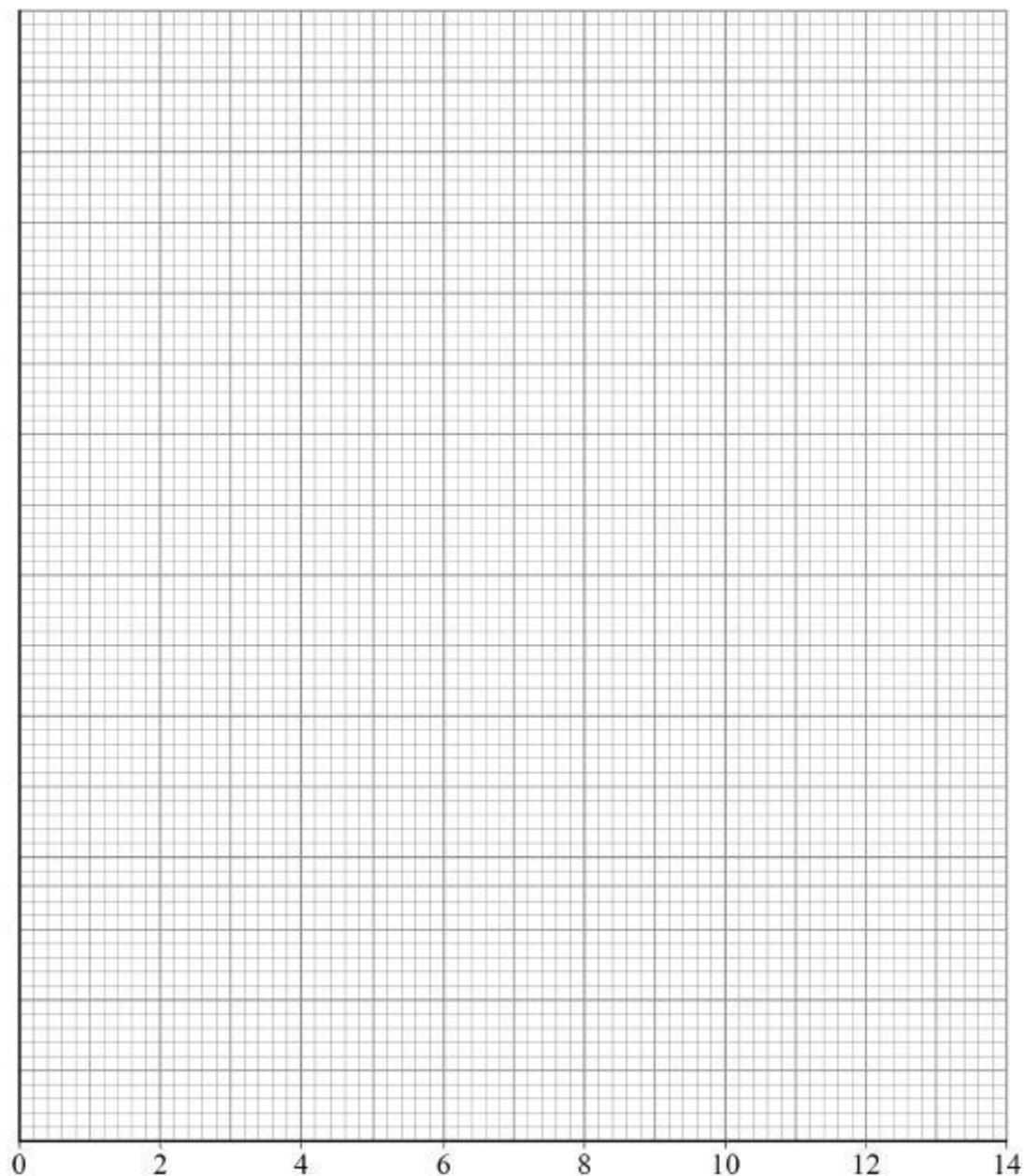

(g) It can be shown that

$$A_n = A_0 \delta^{-n}$$

where A_0 is the amplitude of release of the pendulum
 δ is a constant called the damping factor.

Explain how to find δ from your graph.
You are **not** required to determine δ .

(2)
(Total 15 marks)