

Name of the Student: _____


Max. Marks : 11 Marks

Time : 11 Minutes

Q1.

A circuit is required to amplify the output voltage from a microphone by a factor of 100. The input resistance of the amplifier must be $4.7 \text{ k}\Omega$ to match the internal resistance of the microphone.

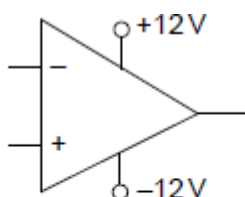- (a) In the space below, complete the circuit diagram of a suitable op-amp amplifier and give suitable resistor values to match the specification. The circuit can be inverting or non-inverting.




_____ 0V

(4)

- (b) The op-amp is powered by a $\pm 12 \text{ V}$ supply. Assuming an ideal op-amp is used, calculate the maximum amplitude of the input signal before the output becomes saturated.

(2)

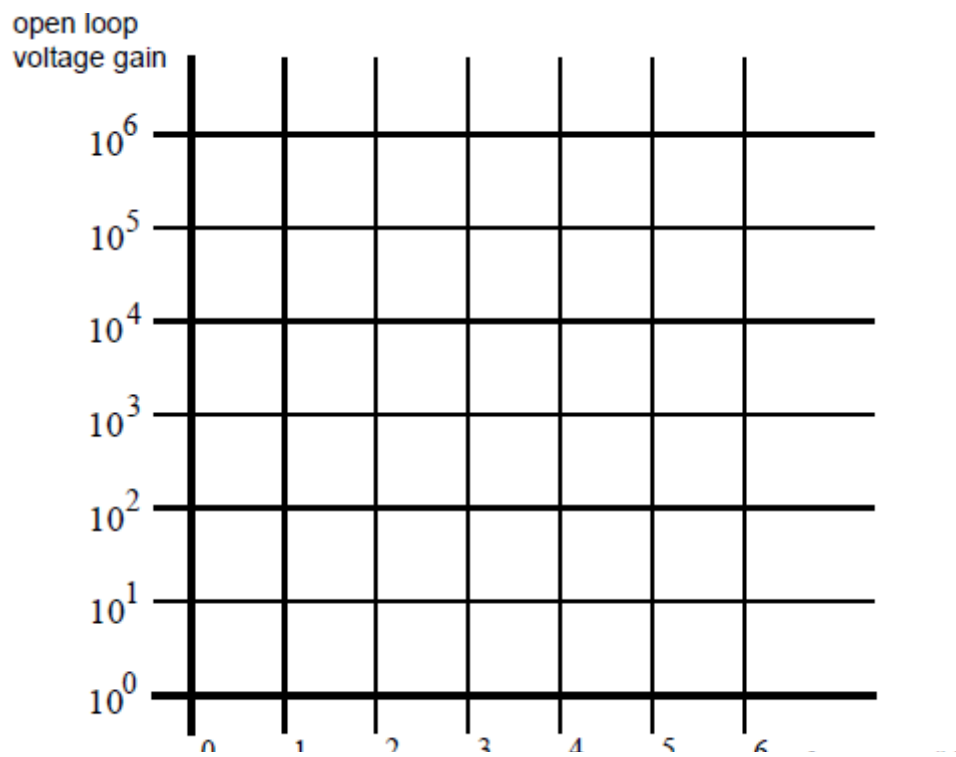- (c) The op-amp has a gain-bandwidth product of 1 MHz . Draw on the graph below how the open loop voltage gain of the op-amp varies with frequency.



(3)

- (d) Calculate the frequency above which the voltage gain of the amplifier is less than 100.

(2)

(Total 11 marks)