


Name of the Student: _____

Max. Marks : 23 Marks

Time : 23 Minutes

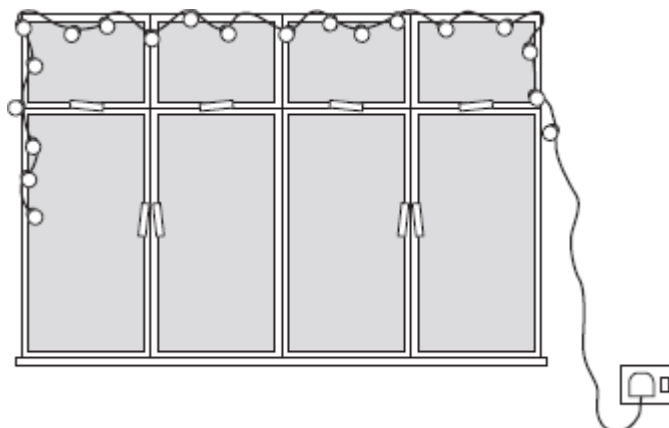Q1.

A set of lights consists of 20 lamps connected in series to the 230 V mains electricity supply.



- (a) When the lights are switched on and working correctly, the current through each lamp is 0.25 A.

- (i) What is the total current drawn from the mains supply?

(1)

- (ii) Calculate the charge passing through **one** of the lamps in 5 minutes.

Show clearly how you work out your answer and give the unit.

Total charge = _____

(3)

- (b) One of the lamps in the set is a fuse lamp. This contains a filament which melts if a fault occurs. A short time after the lights are switched on, a fault causes the filament inside the fuse lamp to melt and all the lamps go out.

The householder cannot find another fuse lamp so connects a piece of aluminium foil across the contacts inside the fuse lamp holder.

When switched on, the nineteen remaining lamps work.

What the householder has done is dangerous.

Explain why.

(2)


(Total 6 marks)

Q2.

The diagram shows a strain gauge, which is an electrical device used to monitor a changing force.

Applying a force to the gauge causes it to stretch.

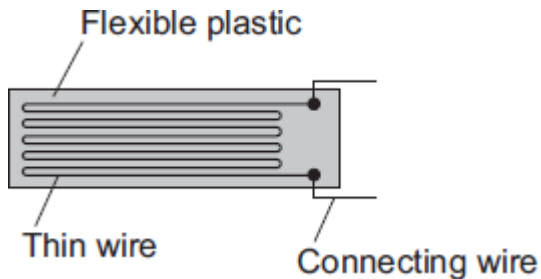This makes the electrical resistance of the wire change.



- (a) (i) Using the correct symbols, **add** to the diagram to show how a battery, an ammeter and a voltmeter can be used to find the resistance of the strain gauge drawn above.

(2)

- (ii) When in use, the strain gauge is always connected to a d.c. power supply, such as a battery.

How is a d.c. (direct current) power supply different from an a.c. (alternating current) power supply?

(1)

- (b) Before any force is applied, the unstretched gauge, correctly connected to a 3.0 V battery, has a current of 0.040 A flowing through it.

- (i) Calculate the resistance of the unstretched gauge.

Show clearly how you work out your answer.

Resistance = _____ Ω

(2)

- (ii) Stretching the gauge causes the current flowing through the gauge to decrease.

What happens to the resistance of the gauge when it is stretched?

(1)


- (iii) What form of energy is stored in the gauge when a force is applied and the gauge stretches?

(1)


(Total 7 marks)

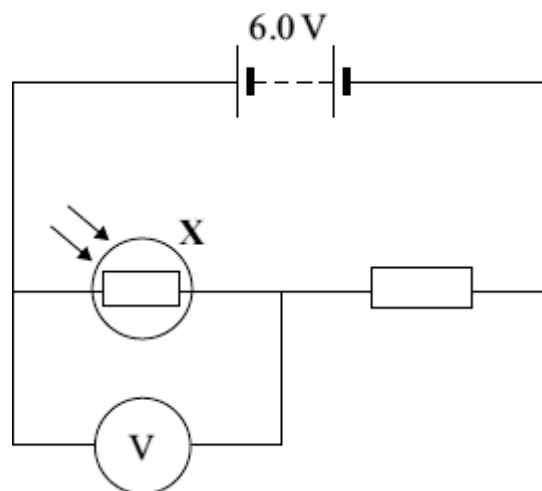Q3.

The diagram shows a simple light-sensing circuit.



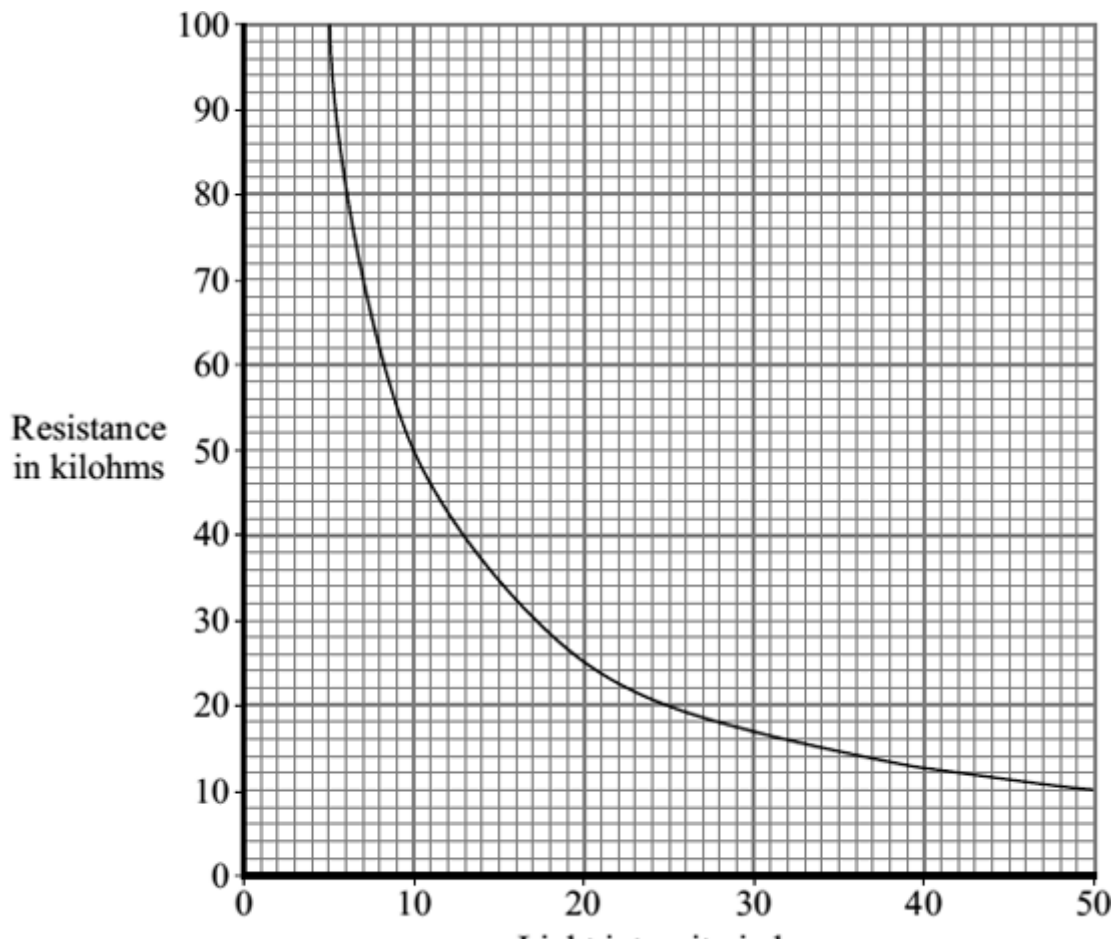- (a) The graph, supplied by the manufacturer, shows how the resistance of the component labelled **X** varies with light intensity.



(i) What is component X?

(1)

(ii) Use the graph to find the resistance of component X when the light intensity is 20 lux.

(1)

(iii) When the light intensity is 20 lux, the current through the circuit is 0.0002 A.

Calculate the reading on the voltmeter when the light intensity is 20 lux.

Show clearly how you work out your answer.

Voltmeter reading = _____ volts

(2)


(b) Use the grid below to show how the voltmeter reading in the light-sensing circuit varies with light intensity.

(i) Add a suitable scale to the y-axis (vertical axis).

(1)

(ii) Complete the sketch graph by drawing a line on the grid to show how the voltmeter

reading will vary with light intensity.

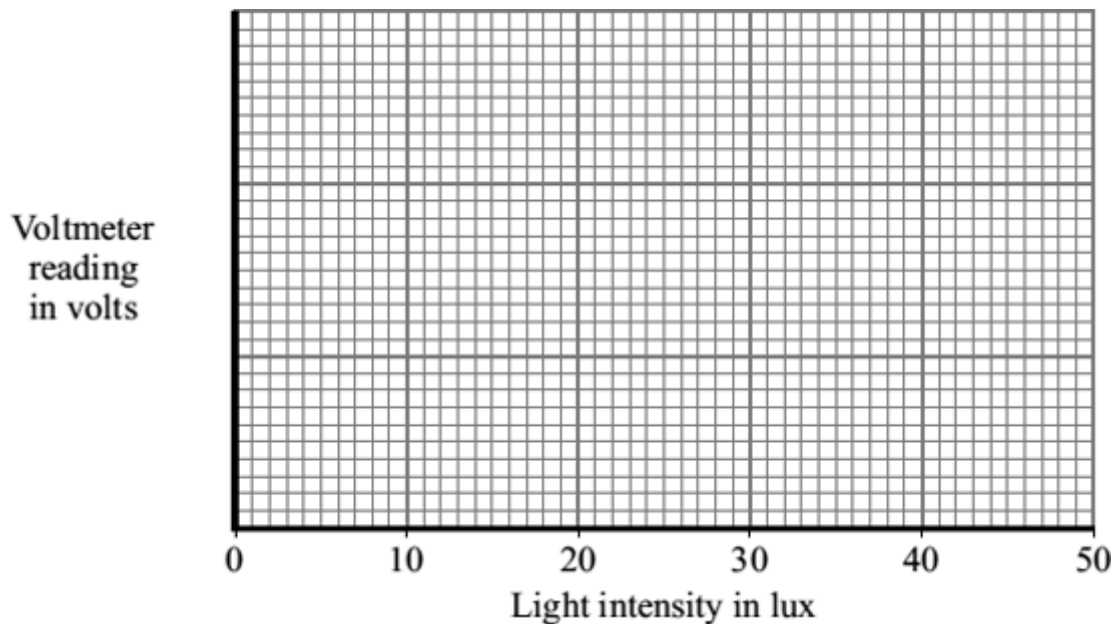

(2)

- (c) The following passage is taken from the technical data supplied for component **X** by the manufacturer.

For any given light intensity, the resistance of this component can vary by plus or minus 50% of the value shown on the **graph of light intensity and resistance**.

- (i) Calculate the maximum resistance that component **X** could have at 20 lux light intensity.

Maximum resistance = _____ kilohms

(1)

- (ii) Explain why this light-sensing circuit would **not** be used to measure values of light intensity.

(2)

(Total 10 marks)